

Simulation Exercise

- Q1 a) Write the netlist for the lowpass filter shown in Fig.1. Run the simulation to obtain frequency response of the filter and verify the cut-off frequency and gain for $V_{in} = 4V_{p-p}$. Sweep the frequency in the appropriate range.
- b) Change value of capacitor C to $0.47\mu F$ and R_2 to $6.8K\Omega$. See the effect.

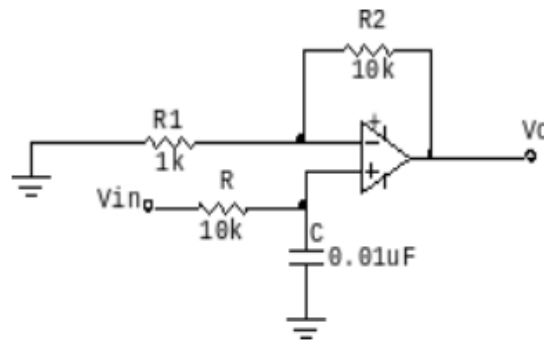


Figure 1

- Q2 a) Write the netlist for the highpass filter shown in Fig.1. Run the simulation to obtain frequency response of the filter and verify the cut-off frequency and gain for $V_{in} = 4V_{p-p}$. Sweep the frequency in the appropriate range.
- b) Change value of capacitor C to $0.47\mu F$ and R_2 to $6.8K\Omega$. See the effect.

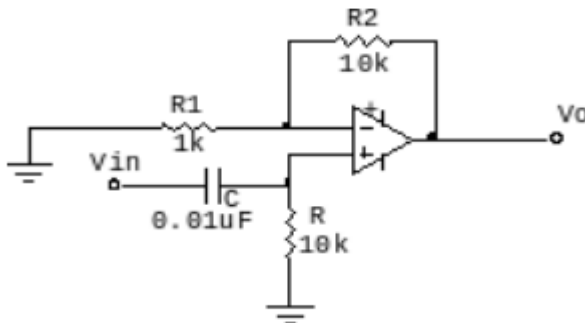


Figure 2

- Q3 a) Write the netlist for the band pass filter shown in Fig.3. Run the simulation to obtain frequency response of the filter and verify the centre frequency and gain for $V_{in} = 4V_{p-p}$. Sweep the frequency in the appropriate range.
- b) Change value of capacitor C_1 to $0.47\mu F$ and R_2 to $6.8K\Omega$. See the effect. Now change C_2 to $0.1\mu F$ and see the effect.

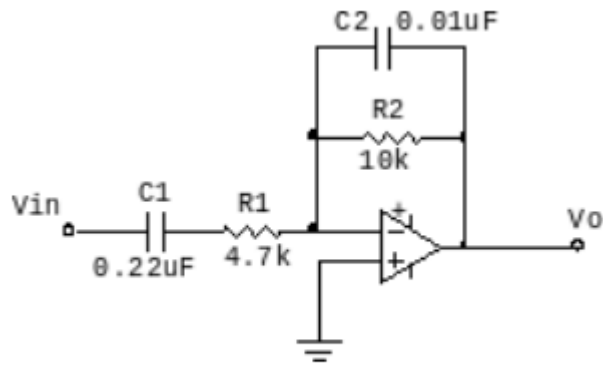


Figure 3

- Q2. a) Design a Butterworth low pass filter for cut-off frequency 15 KHz and pass band gain of 8. Write ngspice netlist, run the simulation and verify the filter specifications.
- b) Design a Butterworth high pass filter for cut-off frequency 15 KHz and pass band gain of 8. Write ngspice netlist, run the simulation and verify the filter specifications.
- c) Design a band pass filter with centre frequency of 5Hz and gain of 8. Write ngspice net list, run the simulation and verify the filter specifications.