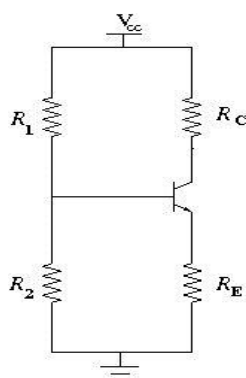


Experiment No 7: BJT biasing Simulation Exercise

Q1 Write the net list for the biasing network shown in Fig. 4.



We will use Transistor, BC547, $R_1 = 47 \text{ k}$, $R_2 = 5.6 \text{ k}$, $R_C = 1.8 \text{ k}$, $R_E = 1 \text{ k}$.

- Tabulate the following quantities: V_{CE} , I_C , I_E , I_B , and V_E .
- Plot the DC load line and locate the operating point.

Hint: To plot DC load line you have to find the intercepts on X and Y axes by making $I_C=0$ for X axis intercept and by making $V_{CE}=0$ for Y axis intercept in the following equation.

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

- Apply input signal of 50mVp-p through a capacitor of 10 μ F into the base.

Observe the output voltage with respect to input voltage. Comment on the output amplitude and the wave shape.

- Replace the transistor by SL100 and tabulate the values of V_{CE} , I_C , I_E , I_B , and V_E .
- Repeat steps a, b, c, and d for

- BC547, $R_1 = 47 \text{ k}$, $R_2 = 5.6 \text{ k}$, $R_C = 1.8 \text{ k}$, $R_E = 1 \text{ k}$
- BC547, $R_1 = 47 \text{ k}$, $R_2 = 18 \text{ k}$, $R_C = 1.8 \text{ k}$, $R_E = 1 \text{ k}$
- BC547, $R_1 = 68 \text{ k}$, $R_2 = 5.6 \text{ k}$, $R_C = 4.7 \text{ k}$, $R_E = 1 \text{ k}$
- BC547, $R_1 = 68 \text{ k}$, $R_2 = 33 \text{ k}$, $R_C = 4.7 \text{ k}$, $R_E = 1 \text{ k}$

Sr. No	BC547, $R_1 =$ $R_2 =$ $R_C =$ $R_E =$	SL100 $R_1 =$ $R_2 =$ $R_C =$ $R_E =$	BC547, $R_1 =$ $R_2 =$ $R_C =$ $R_E =$	BC547 $R_1 =$, $R_2 =$, $R_C =$, $R_E =$ =	BC547 $R_1 =$, $R_2 =$, $R_C =$, $R_E =$ =	BC547 $R_1 =$, $R_2 =$, $R_C =$, $R_E =$ =